



ENGR 305

Voltage Regulation

Rectifier Circuits


September 16, 2025

Voltage regulation

- A **voltage regulator** is a circuit designed to provide a constant dc voltage between its input and output terminals.
- The output voltage must remain as constant as possible in spite of
 - Changes in the load current from the regulator output terminal
 - Changes in the dc power supply that feeds the regulator circuit
- The forward-voltage drop of the diode remains almost constant at 0.7 V while the current varies by relatively large amounts
 - Thus, a forward-biased diode can make a simple voltage regulator.
- We can obtain regulated voltages greater than 0.7 V by connecting a number of diodes in series.

Voltage regulation – example 4.6

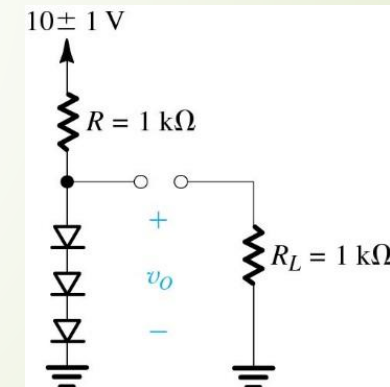- Consider the circuit shown. A string of three diodes is used to provide a constant voltage of about 2.1 V.
- We want to calculate the percentage change in this regulated voltage caused by
 - (a) a $\pm 10\%$ change in the power-supply voltage
 - (b) connection of a $1\text{-k}\Omega$ load resistance



Voltage regulation – example 4.6

- ▶ With no load, the nominal value of the current in the diode string is given by

- ▶ $I = \frac{10 - 2.1}{1k\Omega} = 7.9 \text{ mA}$

- ▶ Each diode will have an incremental resistance of

- ▶ $r_d = \frac{V_T}{I} = \frac{25 \text{ mV}}{7.9 \text{ mA}} = 3.2 \Omega$

- ▶ The three diodes in series will have a total incremental resistance of

- ▶ $r = 3r_d = 9.6\Omega$

Voltage regulation – example 4.6


- This incremental resistance, along with the resistance R , forms a voltage divider whose ratio can be used to calculate the **change in output voltage** due to a $\pm 10\%$ ($\pm 1V$) change in supply voltage.
- The peak-to-peak change in output voltage will be
 - $\Delta v_O = 2 \frac{r}{r+R} = 2 \frac{0.0096 \text{ k}\Omega}{0.0096 \text{ k}\Omega + 1 \text{ k}\Omega} = 19 \text{ mV}$
- Corresponding to the $\pm 1V$ ($\pm 10\%$) change in supply voltage, the output will change by $\pm 9.5 \text{ mV}$ or $\pm 0.5\%$.
- This implies a change of about $\pm 3.2 \text{ mV}$ per diode, making our use of the small-signal model justified.

Voltage regulation – example 4.6

- Connecting a load resistance of $1\text{ k}\Omega$ across the diode string, it draws a current of approximately 2.1 mA .
- The current in the diodes decreases by 2.1 mA , resulting in a decrease in voltage across the diode string given by
 - $\Delta v_O = -2.1 \times r = -2.1\text{ mA} \times 9.6\ \Omega = -20\text{ mV}$
- This implies a voltage decrease across each diode of about 6.7 mV , which does not entirely justify use of the small-signal model.
- Yet, a detailed calculation of the voltage change using the exponential model yields $\Delta v_O = -23\text{ mV}$, which is not significantly different from our result.

Rectifier circuits

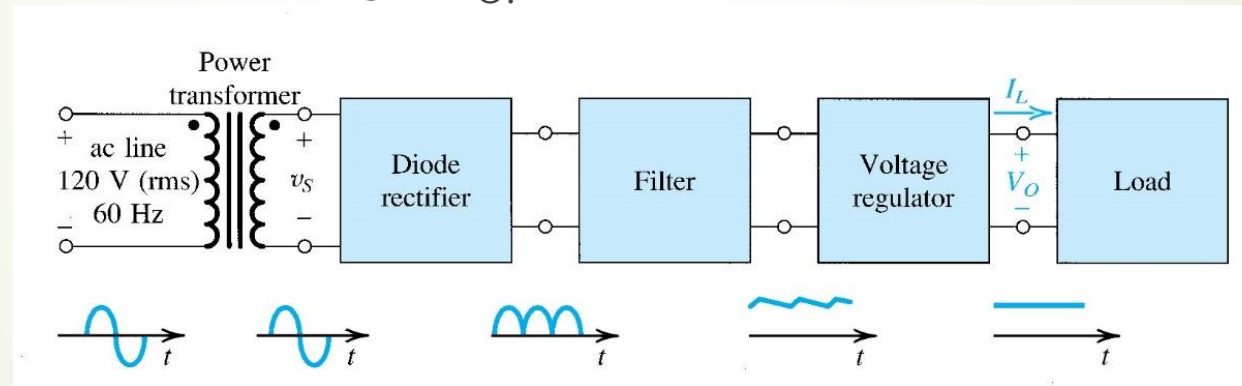- A diode rectifier forms an essential building block of the dc power supplies required to power electronic equipment.
- The power supply is fed from the 120-V (rms) 60-Hz ac line, and it delivers a dc voltage V_O .



Rectifier circuits



- The first block in a dc power supply is the **power transformer**.
 - It consists of two separate coils wound around an iron core that magnetically couples the two windings.
 - The **primary winding**, having N_1 turns, is connected to the 120-V ac supply.
 - The **secondary winding**, having N_2 turns, is connected to the circuit of the dc power supply.
 - An ac voltage v_s of $120(N_2/N_1)$ V (rms) develops between the two terminals of the secondary winding.
- In addition to providing the appropriate sinusoidal amplitude for the dc power supply, the power transformer provides electrical isolation between the electronic equipment and the power-line circuit.

Rectifier circuits

- The *diode rectifier* converts the input sinusoid v_s to a unipolar output, which can have a pulsating waveform.
- Next, the variations in the magnitude of the rectifier output are considerably reduced by the *filter block*.
- The output of the rectifier filter, though much more constant than without the filter, still contains a time-dependent component, called **ripple**.
- To reduce the ripple and to stabilize the magnitude of the dc output against variations caused by changes in load current, we use a *voltage regulator*.

Half-wave rectifier

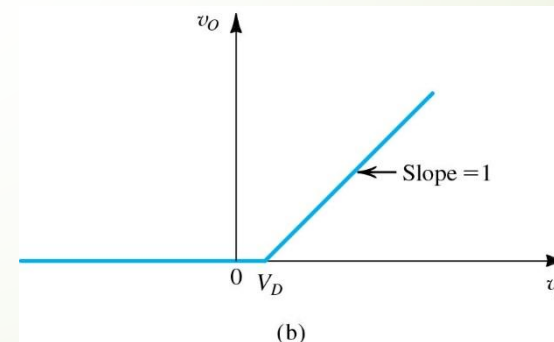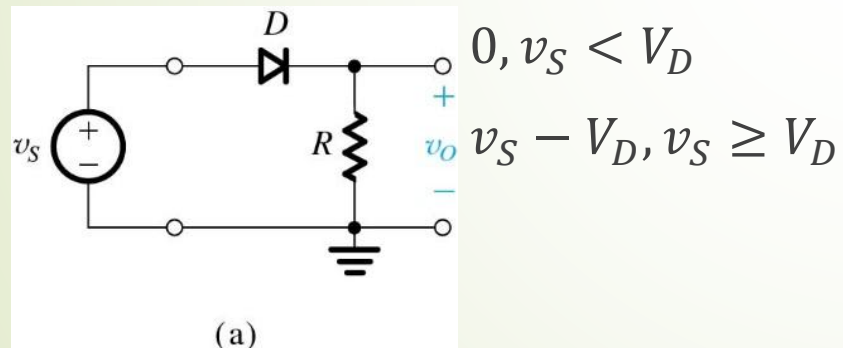
- ▶ The half-wave rectifier uses alternate half-cycles of the input sinusoid.
- ▶ We analyzed the circuit below previously.
- ▶ Now, using the constant-voltage-drop diode model



Transfer characteristic of the circuit

Half-wave rectifier

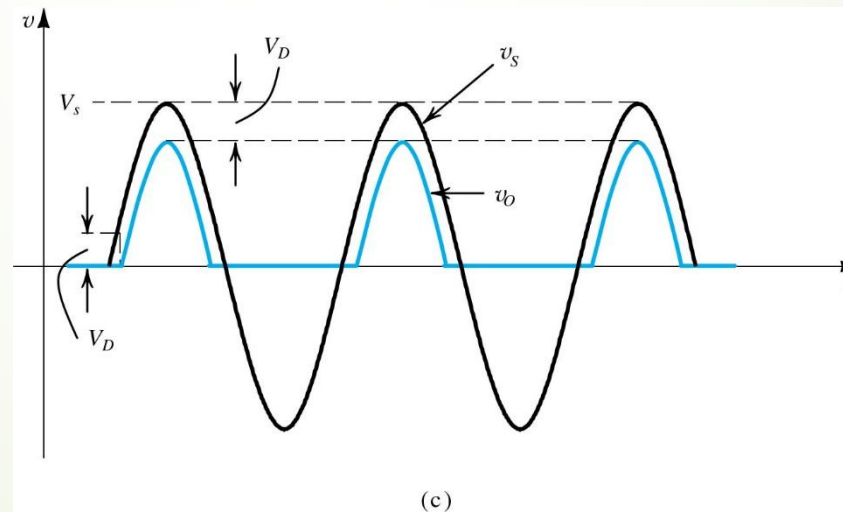- ▶ We assume a forward voltage $V_D = 0.7\text{ V}$
- ▶ The figure shows the output voltage when v_s is a sinusoid.



Half-wave rectifier

- ▶ Two important parameters that are specified in rectifier design
 - ▶ The current-handling capability of the diode or the largest forward current
 - ▶ The **peak inverse voltage** (PIV) that the diode must be able to withstand without breakdown
- ▶ The peak inverse voltage is determined by the largest reverse voltage that is expected to appear across the diode.
- ▶ In the half-wave rectifier circuit, when v_s is negative, the diode will be cut off.
- ▶ The PIV will then be equal to the peak of v_s
 - ▶ $PIV = V_s$
- ▶ It is a good idea in practice to select a diode that has a reverse breakdown voltage at least 50% greater than the expected PIV.