



# ENGR 305

Diodes



September 9, 2025

# Diodes

- In the past we used linear circuit amplification.
- There are many other signal-processing functions that require nonlinear circuits.
  - Generation of dc voltages from an ac power supply
  - Generation of signals of various waveforms
  - Digital logic and memory circuits
- The simplest and most fundamental nonlinear circuit element is the diode.
- We begin with a simplified model, a fictitious element, the ideal diode.
- Then we move on to the silicon junction diode.

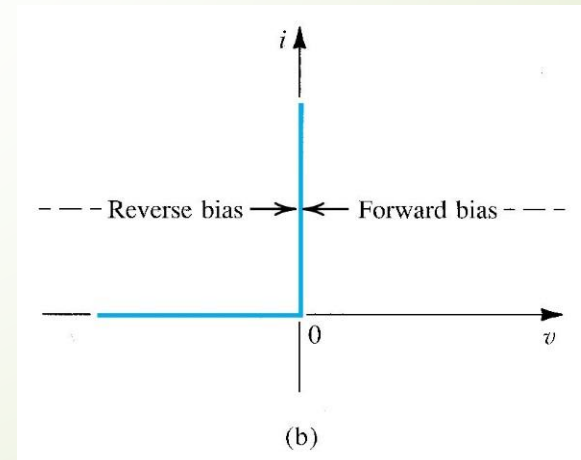
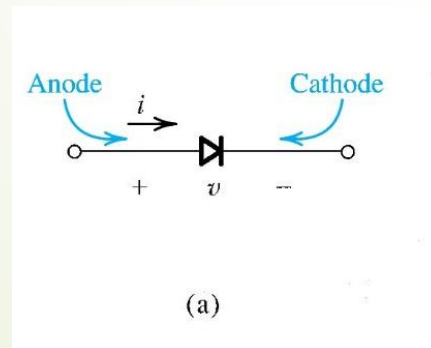
# The ideal diode

- This ideal diode is the most fundamental nonlinear circuit element.
- It is a two-terminal device with the circuit symbol shown in part (a)
- The current-voltage, or  $i$ - $v$ , characteristic, is shown in part (b)



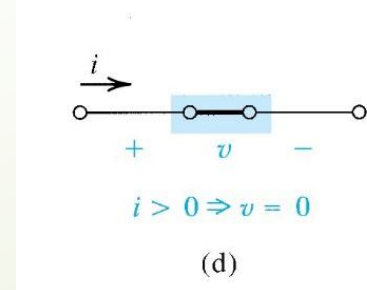
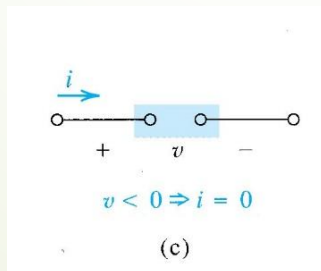
# The ideal diode

- If a negative voltage is applied to the anode with respect to the cathode, no current flows
  - It behaves as an open circuit (part (c) of figure)
  - The diode is **reverse-biased**. The diode is **cut off**.
- If a positive voltage is applied to the anode with respect to the cathode, zero voltage drop appears across the diode.
  - The ideal diode behaves as a short circuit in the forward direction and is **forward-biased** (part (d) of figure) The diode is **on**.




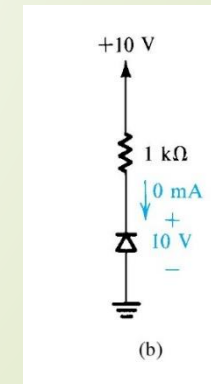
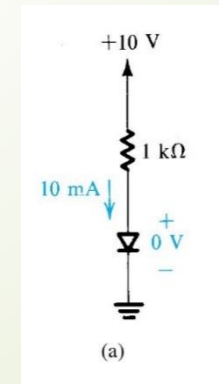
# The ideal diode

- The circuit that is external to the diode must be designed to
  - Limit the forward current through a conducting diode
  - Limit the reverse voltage across a cutoff diode
- The diode in part (a) is conducting
  - The current through it is determined by the +10-V supply and the 1-k $\Omega$  resistor as 10 mA.
- The diode in part (b) is cut off, the current will be zero and the 10-V supply voltage appears as a reverse bias across the diode.
- The positive terminal is the **anode**.
- The negative terminal is the **cathode**.



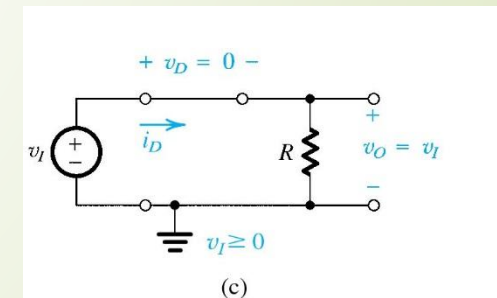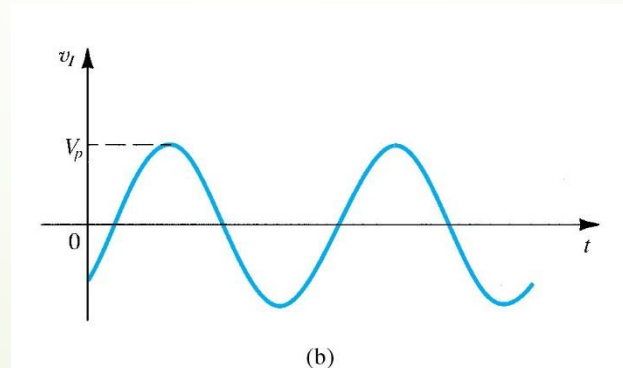
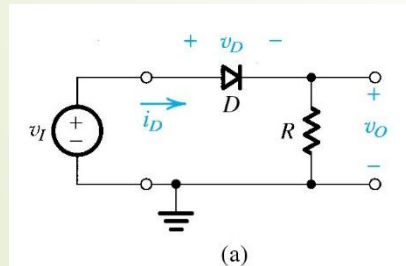
# The rectifier

- The circuit consists of the series connection of a diode  $D$  and a resistor  $R$ .
- Let the input voltage  $v_I$  be the sinusoid shown.
  - During the positive half-cycles of the input sinusoid, the positive  $v_I$  will cause current to flow in the forward direction of the diode.
  - The circuit has the equivalent circuit shown in part (c).


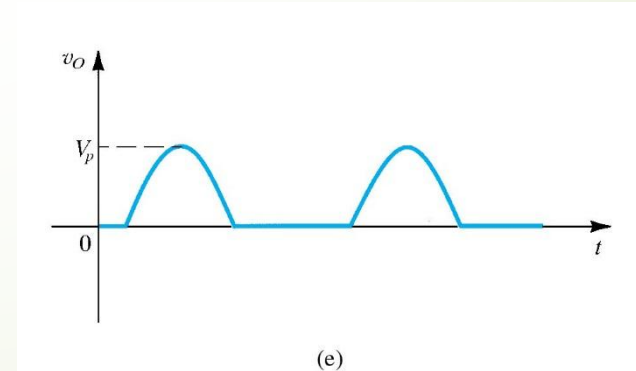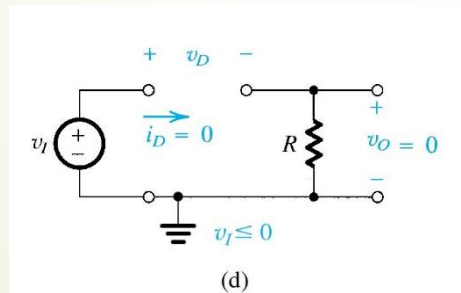
# The rectifier



- During the negative half-cycles of  $v_I$ , the diode does not conduct.
- In this case the equivalent circuit is shown in part (d) and  $v_O$  is zero.
- The output has the waveform shown in part (e).
- While  $v_I$  alternates and has a zero average value,  $v_O$  is unidirectional and has a finite average value or *dc component*.





## Example 4.1

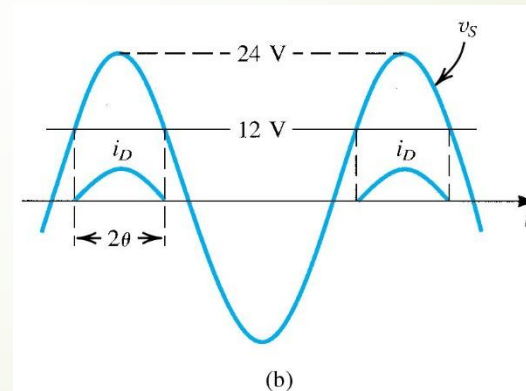
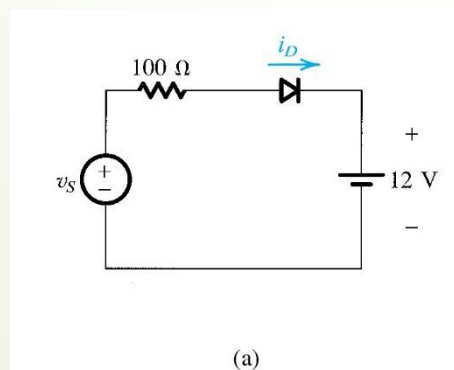
- Part (a) of the figure shows a circuit for charging a 12-V battery. If  $v_s$  is a sinusoid with 24-V peak amplitude, find the fraction of each cycle during which the diode conducts.
- Also find the peak value of the diode current and the maximum reverse-bias voltage that appears across the diode.





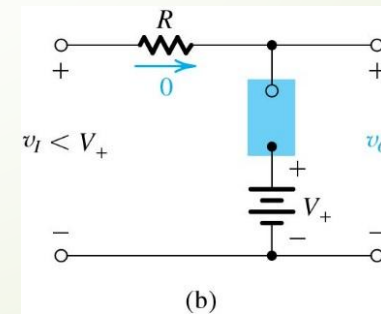
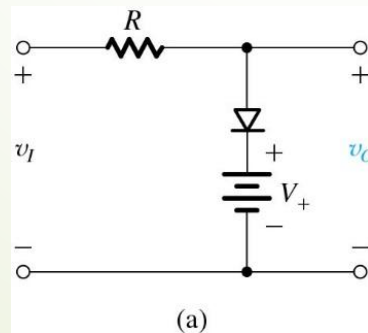
# Limiting and protecting circuits

- A rearrangement of the circuit from the previous example results in a simple limiter circuit as shown in (a). Limiter circuits limit voltage excursions.
- When the input voltage  $v_I$  is below  $V_+$ , the diode is off and an open circuit.
- No current flows through the resistor  $R$ , and  $v_O = v_I$ .
- The equivalent schematic is shown in part (b).



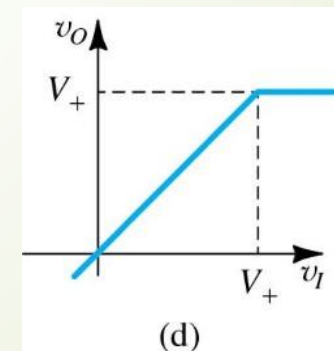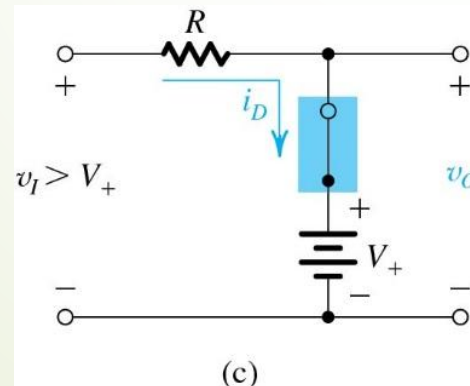
# Limiting and protecting circuits

- When the input  $v_I$  exceeds  $V_+$ , the diode turns on, resulting in the circuit shown in part (c), where  $v_O = V_+$ .
- The circuit keeps  $v_O$  from exceeding the upper limit established by  $V_+$ .
  - The input-output characteristic is shown in part (d) of the figure.
  - When on the diode conducts a current  $i_D = \frac{v_I - V_+}{R}$ .



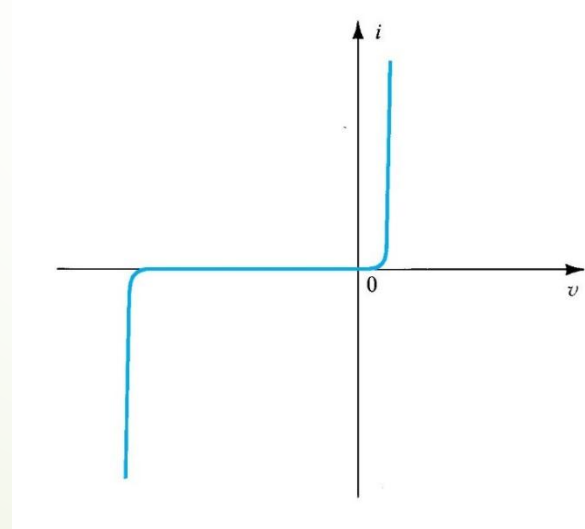
# Terminal characteristics of junction diodes

- ▶ The most common implementation of the diode uses a *pn* junction.
  - ▶ We consider the *i-v*, or current-voltage, characteristics of the *pn* junction.
  - ▶ The *pn* junction can conduct substantial current in the forward direction.
  - ▶ It conducts almost no current in the reverse direction.


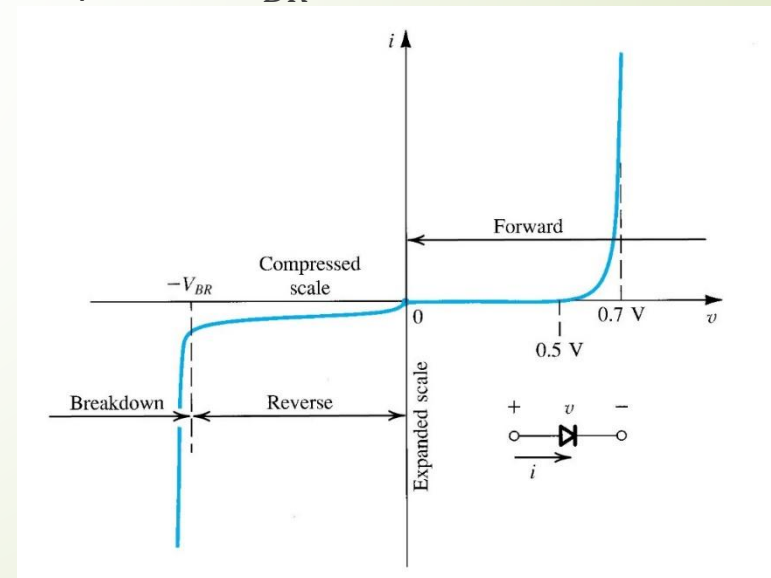
# Terminal characteristics of junction diodes

- ▶ The characteristic curve consists of three distinct regions
  1. The forward-bias region, determined by  $v > 0$
  2. The reverse-bias region, determined by  $v < 0$
  3. The breakdown region, determined by  $v < -V_{BR}$



# The forward-bias region

- ▶ The diode is in the forward-bias region when the terminal voltage  $v$  is positive.
- ▶ In the forward region, the  $i$ - $v$  relationship is approximated by
  - ▶  $i = I_S(e^{v/V_T} - 1)$
- ▶ In this equation,  $I_S$  is a constant for a given diode at a given temperature.
  - ▶ The current  $I_S$  is usually called the **saturation current**.
  - ▶ It is sometimes referred to as the **scale current**.
  - ▶ Doubling the junction area produces a diode with double the value of  $I_S$ .
  - ▶ For “small-signal” diodes, intended for low-power applications,  $I_S$  is on the order of  $10^{-15}$  A.

# Forward-bias region

- The voltage  $V_T$  is called the **thermal voltage** and is given by
  - $V_T = \frac{kT}{q}$
  - Where  $k$  = Boltzmann's constant =  $8.62 \times \frac{10^{-5} \text{ eV}}{\text{K}} = 1.38 \times 10^{-23} \text{ joules/kelvin}$
  - $T$  = absolute temperature in kelvins =  $273 + \text{temperature in } ^\circ\text{C}$
  - $q$  = the magnitude of electronic charge =  $1.60 \times 10^{-19} \text{ coulomb}$
  - Substituting these gives a value  $V_T = 0.0862T, \text{ mV}$
  - At room temperature, we have  $V_T \cong 25 \text{ mV}$

# Forward-bias region

- ▶ For appreciable current  $i$  in the forward direction, where  $i \gg I_S$ , we can approximate it by the exponential relationship
  - ▶  $i \cong I_S e^{v/V_T}$
- ▶ We can rearrange this equation so that it is in the logarithmic form
  - ▶  $v = V_T \ln \frac{i}{I_S}$
- ▶ The exponential relationship of the current  $i$  to the voltage  $v$  holds over a span of many decades of current.



# Forward-bias region


- ▶ Applying the  $i$ - $v$  relationship to a diode with current  $I_1$  and voltage  $V_1$ 
  - ▶  $I_1 = I_S e^{V_1/V_T}$
- ▶ If the voltage is  $V_2$ , the diode current  $I_2$  will be
  - ▶  $I_2 = I_S e^{V_2/V_T}$
- ▶ Taking the ratio of  $I_2$  to  $I_1$ 
  - ▶  $\frac{I_2}{I_1} = e^{(V_2 - V_1)/V_T}$
- ▶ This can be rewritten as  $V_2 - V_1 = V_T \ln \frac{I_2}{I_1}$
- ▶ Putting this in terms of base-10 logarithms,  $V_2 - V_1 = 2.3V_T \log \frac{I_2}{I_1}$

# Forward-bias region

- The equation states that for a decade change in current, the diode voltage drop changes by  $2.3V_T$ , which is approximately 60 mV.
- Referring to the  $i$ - $v$  characteristic in the forward region, the current is negligibly small for voltages less than 0.5 V.
  - This voltage is referred to as the **cut-in voltage**.
- For a “fully conducting” diode, the voltage drop lies in a narrow range, 0.6-0.8 V.
- We use a simple “model” for the diode where we assume that a conducting diode has approximately a 0.7-volt drop across it.
- This 0.7-volt model applies to silicon diodes.
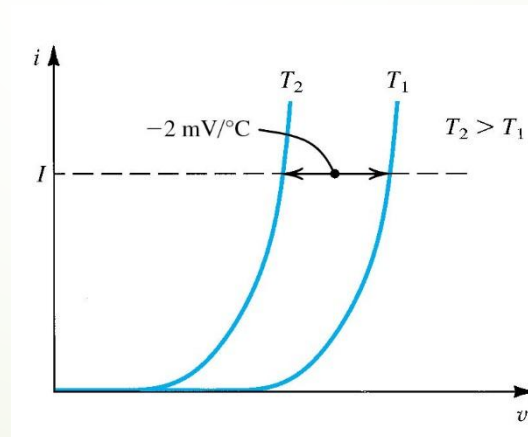
# Temperature dependence of $i$ - $v$ curve

- Both  $I_S$  and  $V_T$  are functions of temperature
- The forward  $i$ - $v$  characteristic varies with temperature
- At a given constant diode current, the voltage drop across the diode decreases by roughly 2 mV for every 1°C increase in temperature.



## Reverse-bias region

- ▶ When  $v$  becomes negative, the diode enters the reverse-bias region of operation.
- ▶ If the negative voltage  $v$  becomes a few times larger than  $V_T$  in magnitude, the exponential term becomes negligible compared to unity.
  - ▶ The diode current is then  $i \cong -I_S$
- ▶ The current in the reverse direction is constant.
- ▶ This is where the term *saturation current* comes from.

# Breakdown region

- The diode enters the breakdown region when the magnitude of the reverse voltage exceeds a threshold value that is specific to the particular diode
  - It is called the **breakdown voltage, or  $V_{BR}$**
- In the breakdown region, the reverse current increases rapidly, and the increase in voltage drop is very small.
- Diode breakdown is normally not destructive, as long as the power dissipated in the diode is limited to a “safe” level.
- The safe values of current and power dissipation are specified on the device data sheets.