




ENGR 305

Voltage Rectifier Circuits

September 18, 2025

The full-wave rectifier

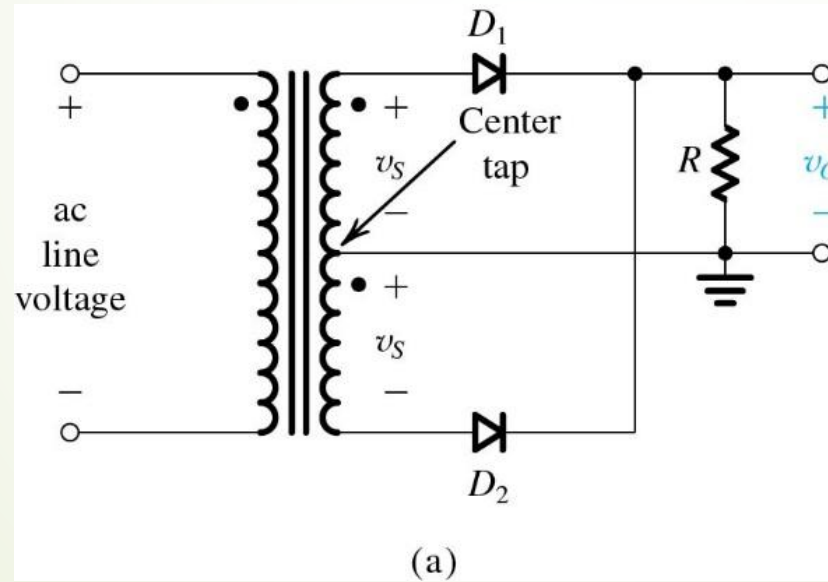- We consider the full-wave rectifier using a transformer with a center-tapped secondary winding.



The full-wave rectifier


- ▶ The full-wave rectifier uses both halves of the input sinusoid.
 - ▶ It inverts the negative halves of the sine wave to produce a unipolar output.
- ▶ One possible implementation (as shown) has a **center-tapped** secondary winding.
- ▶ For the case when the input line voltage (feeding the primary) is positive:
 - ▶ Both signals labeled v_s will be positive.
 - ▶ Diode D_1 will conduct and D_2 will be reverse biased.
 - ▶ The current through D_1 will flow through R and back to the center tap of the secondary.
 - ▶ The circuit then behaves like a half-wave rectifier.

Full-wave rectifier


- During the negative half-cycle of the ac line voltage, both voltages labeled v_s will be negative.
 - Then D_1 will be cut off while D_2 will conduct.
 - The current conducted by D_2 will flow through R and back to the center tap.
 - The circuit again behaves like a half-wave rectifier.
- Note that for both half cycles the current through R always flows in the same direction.
 - This causes the resulting v_o to be unipolar.
 - We again use the constant-voltage-drop model for the diode ($V_D = 0.7\text{ V}$)

Full-wave rectifier

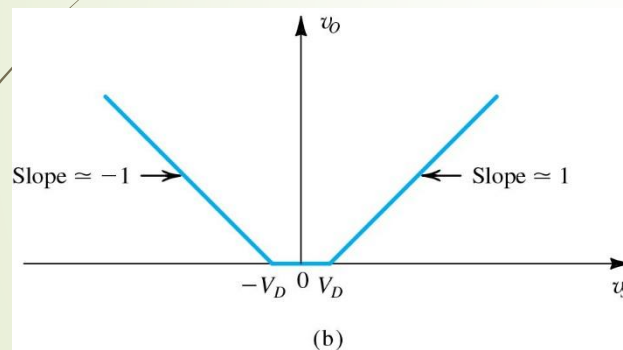- The resulting v_o is unipolar as shown.
- The transfer characteristic is also shown.



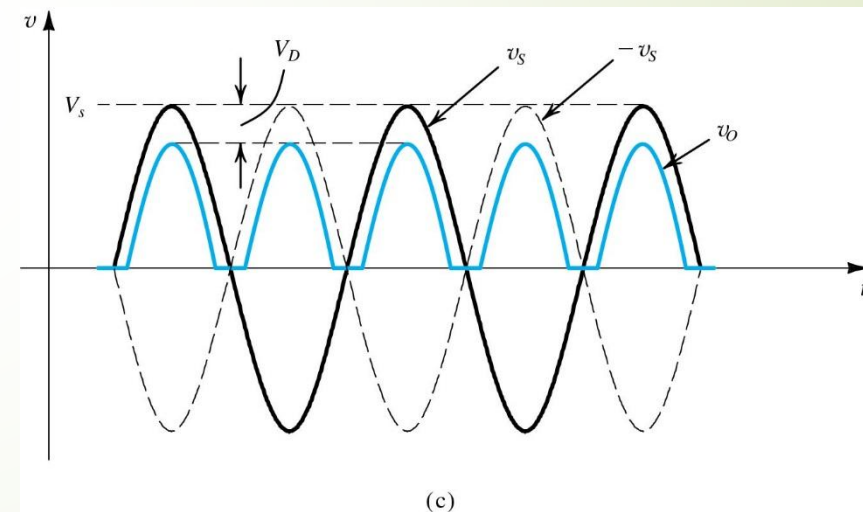Transfer characteristic for full-wave rectifier.




Full-wave rectifier

- ▶ Recalling that the Peak Inverse voltage (PIV) is an important parameter in rectifier design
 - ▶ During the positive half-cycles, D_1 is conducting while D_2 is cut off.
 - ▶ Voltage at the cathode of D_2 is v_o and at its anode is $-v_s$.
 - ▶ The reverse voltage across D_2 will be $(v_o + v_s)$
 - ▶ This reaches its maximum when v_o is at its peak value of $(V_S - V_D)$ and v_s is at its peak value of V_S
 - ▶ Then $PIV = 2V_S - V_D$


The Bridge rectifier

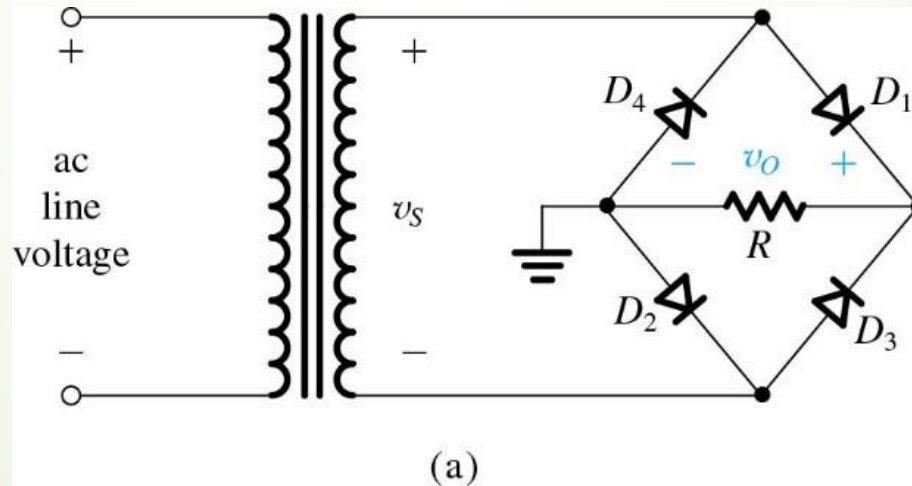- ▶ The bridge rectifier is an alternative implementation to the full-wave rectifier.
- ▶ It does not require a center-tapped transformer.
- ▶ It does require four diodes instead of two diodes.




The bridge rectifier

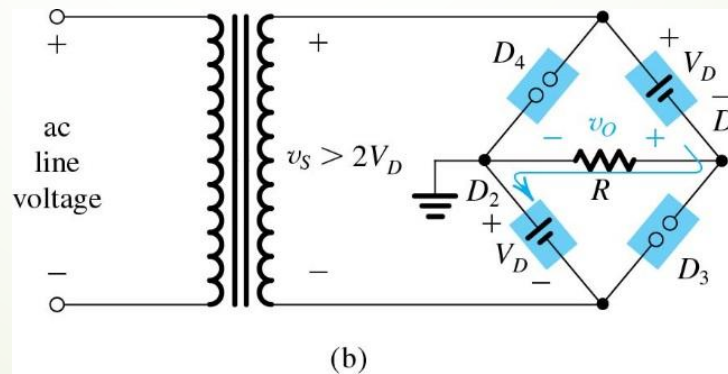- During the *positive* half-cycles of the input voltage, v_s is positive
 - Current is conducted through diode D_1 , resistor R , and diode D_2 .
 - Diodes D_3 and D_4 will be reverse biased.
 - Since there are two diodes in the conduction path, v_o will be lower than v_s by two diode drops.



The bridge rectifier

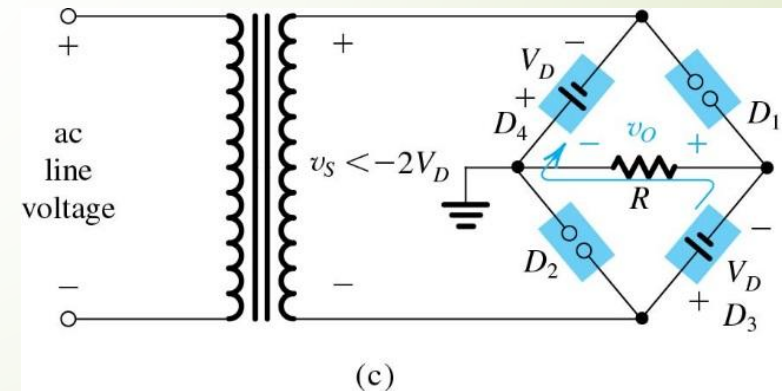- During the *negative* half-cycles of the input voltage, v_s is negative.
 - Thus, $-v_s$ will be positive, forcing current through D_3 , R and D_4 .
 - Diodes D_1 and D_2 will be reverse biased.
 - During both half-cycles, current flows through R in the same direction (from right to left)
 - Then v_o will always be positive.




The bridge rectifier

- ▶ We want to determine the peak inverse voltage (PIV) of each diode.
- ▶ The reverse voltage across D_3 can be found from the loop formed by D_3 , R and D_2
 - ▶ $v_{D3}(\text{reverse}) = v_o + v_{D2}(\text{forward})$
- ▶ The maximum value of v_{D3} occurs at the peak of v_o and is given by
 - ▶ $PIV = V_S - 2V_D + V_D = V_S - V_D$
- ▶ Here the PIV is about half the value for the full-wave rectifier with a center-tapped transformer.


Rectifier with a filter capacitor

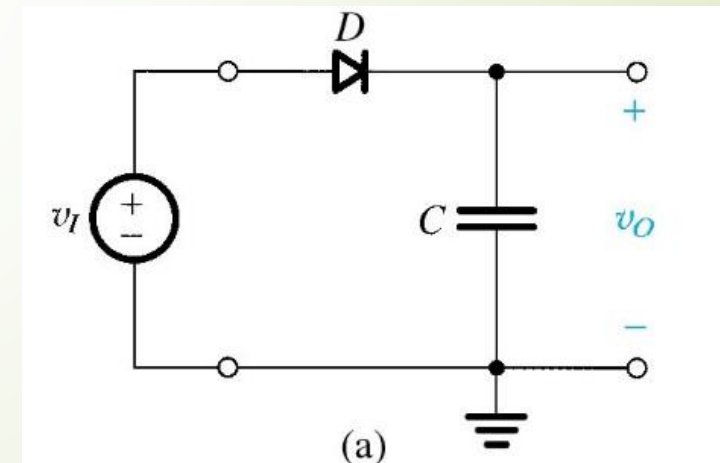- The output voltage waveform of the rectifier circuits is not suitable for a dc power supply.
- A simple way to reduce the variation in the output voltage is to place a capacitor across the load resistor, called a **filter capacitor**.
- We first consider the simple circuit shown.




Rectifier with a filter capacitor

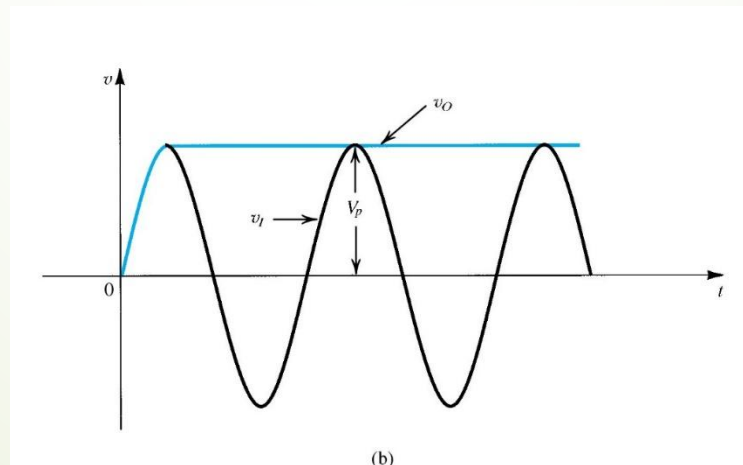- ▶ Let the input v_I be a sinusoid with a peak value V_p
- ▶ Assume the diode to be *ideal*.
- ▶ As v_I goes positive, the diode conducts and the capacitor is charged so that $v_O = v_I$
- ▶ This continues until v_I reaches its peak value V_p . As v_I decreases, the diode becomes reverse biased and the output remains (theoretically) constant at the value V_p .



Rectifier with a filter capacitor


- Consider the more practical circuit with a load resistance R connected across the capacitor.
 - For a sinusoidal input, the capacitor charges to the peak value of input of V_p .
 - Then the diode cuts off, and the capacitor discharges through the load resistance R .
 - The capacitor discharge continues until the time at which v_I exceeds the capacitor voltage.
 - We choose a value for C so that the time constant CR is much greater than the discharge interval.

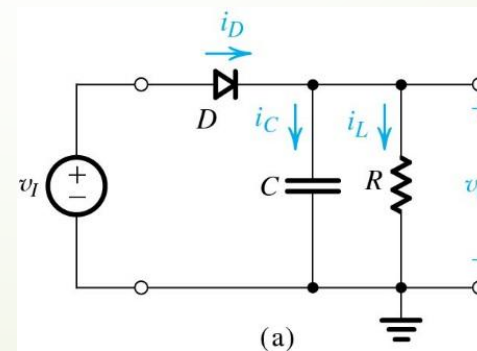

Peak rectifier circuit – voltage and current

Here we see the input and output voltage waveforms under the assumption that $CR \gg T$, where T is the period of the input sinusoid.

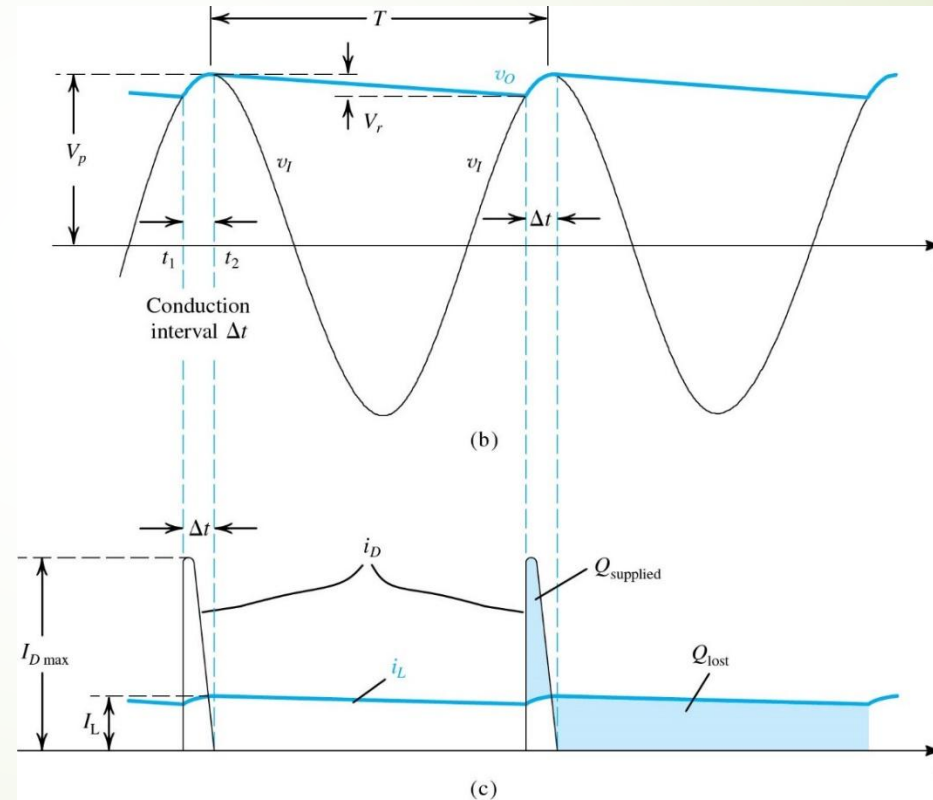The waveforms of the load current, $i_L = v_O/R$ and of the diode current (when it is conducting) $i_D = i_C + i_L = C \frac{dv_I}{dt} + i_L$ are shown.



Peak rectifier circuit - observations

1. The diode conducts for a brief interval, Δt , near the peak of the input sinusoid and supplies the capacitor with charge equal to that lost during the much longer discharge interval, which is approximately equal to T .
2. Assuming an ideal diode, the diode conduction begins at time t_1 , at which the input v_I equals the exponentially decaying output v_O . Conduction stops at t_2 , shortly after the peak of v_I .
3. During the diode-off interval, the capacitor C discharges through R , and so v_O decays exponentially with a time constant CR . The discharge interval begins just past the peak of v_I . At the end of the discharge interval, $v_O = V_p - V_r$, where V_r is the peak-to-peak ripple voltage.
4. When V_r is small, v_O is almost constant and equal to the peak value of v_I . Thus the dc output voltage is approximately equal to V_p .

Peak rectifier circuit

- ▶ Similarly, the current i_L is almost constant, with its dc component given by
 - ▶ $I_L = \frac{V_p}{R}$
- ▶ During the diode-off interval, v_o can be expressed as
 - ▶ $v_o = V_p e^{-t/CR}$
- ▶ At the end of the discharge interval we have
 - ▶ $V_p - V_r \cong V_p e^{-T/CR}$
- ▶ Now, since $CR \gg T$, we can use the approximation $e^{-T/CR} \cong 1 - T/CR$ to get
 - ▶ $V_r \cong V_p \frac{T}{CR}$
- ▶ To keep V_r small we must select a capacitance C so that $CR \gg T$.

Peak rectifier circuit

- The **ripple voltage** V_r in the previous equation can be expressed in terms of the frequency $f = 1/T$ as
 - $V_r = \frac{V_p}{fCR}$
- Using the previous expression for I_L we can express V_r as
 - $V_r = \frac{I_L}{fC}$
- Assuming that the diode conduction ceases almost at the peak of v_I , we can determine the **conduction interval** Δt from
- $V_p \cos(\omega \Delta t) = V_p - V_r$ where $\omega = 2\pi f = 2\pi/T$ is the angular frequency of v_I .

Peak rectifier circuit

- Since $(\omega\Delta t)$ is a small angle, we can use the approximation $\cos(\omega\Delta t) \cong 1 - \frac{1}{2}(\omega\Delta t)^2$
 - Which gives $\omega\Delta t = \sqrt{2V_r/V_p} \xrightarrow{\text{yields}} \Delta t = \frac{T}{2\pi} \sqrt{\frac{2V_r}{V_p}}$
 - We note that when $V_r \ll V_p$ the conduction angle $\omega\Delta t$ will be small.
- Another interpretation is that the charge supplied by the diode to the capacitor during the conduction interval must equal the charge that the capacitor loses during the discharge interval.
- The average capacitor, diode and load currents are related by $i_{Cav} = i_{Dav} - I_L$
- Then, the supplied charge is $Q_{supplied} = i_{Cav}\Delta t \cong (i_{Dav} - I_L) \frac{T}{2\pi} \sqrt{\frac{2V_r}{V_p}}$
- The lost charge is $Q_{lost} = CV_r = I_L T$

Peak rectifier circuit

- Equating the equations for supplied charge and lost charge, the average diode current during conduction is

- $$i_{Dav} = I_L \left(1 + \pi \sqrt{2 V_p / V_r} \right)$$

- To select an appropriate diode, we must find the peak value of diode current.

- We evaluate the current equation at the onset of conduction ($t = -\Delta t$ where $t = 0$ at the peak)

- $$I_{Dmax} = I_L \left(1 + 2\pi \sqrt{2 V_p / V_r} \right)$$

- From these two equations, we see that for $V_r \ll V_p$, $i_{Dmax} \cong 2i_{Dav}$

- This correlates with the fact that the waveform of i_D is almost a right-angle triangle.