

ENGR 305 – Lab #9

2 weeks

NMOS Common-Source Amplifier

OBJECTIVES:

To study an NMOS-based common-source (CS) amplifier by:

- Completing the DC and small-signal analysis based on its theoretical behavior.
- Simulating it to compare the results with the paper analysis.
- Implementing it in an experimental setting, taking measurements, and comparing its performance with theoretical and simulated results.
- Measuring its output resistance.
- Qualitatively seeing the impact of transistor-to-transistor variations.

MATERIALS:

- Laboratory setup, including breadboard.
- 1 enhancement-type NMOS transistor (e.g., 2N7000)
- 3 large (e.g., 47- μ F) capacitors
- Several resistors of varying sizes
- Wires

PART I: DESIGN AND SIMULATION

Design the amplifier to achieve a small-signal gain of at least $A_v = -5$ V/V. Use supplies of $V_+ = +15$ V, $R_{sig} = 50\ \Omega$, $R_L = 10\text{ k}\Omega$, $R_G = 10\text{ k}\Omega$, and design the circuit to have $I_D = 1$ mA. Obtain the datasheet for the NMOS transistor that will be used. In your lab book, perform the following:

DC Operating Point Analysis (Assume for your calculations that $\lambda = 0.0146/\text{V}$, $k_n = 1.08\text{ mA/V}^2$, and $V_{tn} = 1.45\text{ V}$.)

- Sketch a DC model of the circuit in your lab book, replacing the three “large-valued” coupling capacitors C_{C1} , C_{C2} , C_S by open circuits (for simplicity you may also omit v_{sig} , R_{sig} , and R_L). What is the DC current through R_G ?
- Based on the information just given, you have enough information to calculate $V_{OV} = V_{GS} - V_{tn}$. What is its value? What is the value of g_m ? What is V_{GS} ? Remember: Your actual transistor will have a value of V_{tn} that will vary from its nominal value, which will alter your measurement results slightly!
- Calculate r_o .
- You now have enough information to calculate R_S . Show your calculation. Is the value you calculate for R_S available? Can you achieve the value by combining resistors?

- Note: At this stage we know neither V_{DS} nor R_D .

AC Analysis

- Sketch a small-signal model of the circuit in your lab book, replacing the transistor with its small-signal model, replacing the capacitors with short circuits (what happens to R_S ?), and replacing V_+ with an AC ground. What happens to V_- ? Label the gate of the transistor as v_i , i.e., the small-signal voltage at the input.
- What is the ratio of v_o/v_{sig} ? How would you approximate it in further calculations?
- Derive an expression for $A_v = v_o/v_i$. What is the value of R_D that produces a small-signal voltage of *at least* $A_v = -5$ V/V? Is the value you calculated for R_D available? Can you achieve this value by combining resistors?
- What is the DC voltage at the drain? Does this satisfy the assumption that the transistor should be operating in the saturation region? Explain.
- What is the output resistance, R_o ?

Simulation

- Simulate your circuit. Use capacitor values $C_{C1} = C_{C2} = C_S = 47 \mu\text{F}$, and the values of R_S and R_D based on your preceding calculations. Use a 10-mV_{pk-pk}, 1-kHz sinusoid with no DC component applied as v_{sig} . This voltage source is the same as used in Lab 3:

Right-click on voltage source and click on *advanced*.

- Choose SINE:
 - Amplitude – 5 (V)
 - Frequency – 1000 (Hz)

Adding the Spice model directive for the 2N7000:

`.model 2N7000 NMOS(kp=1.08m Vto=1.45 lambda=0.0146)`

How to use it:

1. Add an NMOS component to your schematic
 - a. Right-click the NMOS symbol in the component toolbar.
 - b. Place the generic nmos symbol (NMOS) on your schematic.
2. Edit the diode's properties.
 - a. Ctrl + Right-click on the NMOS symbol.
 - b. In the "Value" field, change the name from NMOS to 2N7000.
 - c. Click OK.
3. Add the Spice model directive.
 - a. Go to Edit->Spice Directive.
 - b. Enter the .model line from above into the dialog box.
 - c. Place the directive anywhere on the schematic.

When you run the simulation, LTSpice will recognize the .model directive and apply the specified parameters to any NMOS component named 2N7000.

- From your simulation, report the DC values of V_{GS} , V_{DS} , and I_D . How closely do they match your calculations? (Remember: The simulator has its own more-complex model of the real transistor, so there should be some small variations.)
- From your simulation, report A_v . How closely does it match your calculations?

PART 2: PROTOTYPING

- Assemble the circuit onto your breadboard using the specified component values and those just calculated. Note that R_{sig} represents the output resistance of the function generator, and therefore you should **not** include it in your circuit.

PART 3: MEASUREMENTS

- *DC bias point measurement:* Using a digital multimeter, measure the DC voltages of your circuit at the gate (V_G), source (V_S), and drain (V_D) of your transistor.
- *AC measurement:* Using a function generator, apply to your circuit a 10-mV_{pk-pk}, 1-kHz sinusoid with no DC component. (*Note:* Some function generators allow only inputs as small as 50 mV_{pk-pk}. If this is the case, use that value instead.)
- Using an oscilloscope, generate plots of v_o and v_i vs. t .
- *Output resistance R_o :* Replace R_L with a 1-M Ω resistor and repeat the AC measurement. What is the amplitude of the output waveform? Adjust R_L until you find a value such that the amplitude of the output waveform is approximately 50% of what it was for the 1-M Ω load. This new value of R_L is the output resistance R_o . How does it compare to the value you calculated earlier in Step 2? *Hint:* It cannot be greater than the value of R_D .
- *Further exploration:* What happens to the shape of the output signal as you increase the amplitude of the input signal, e.g., to 1 V_{pk-pk}? At what input amplitude do you begin to see significant distortion? Can you explain this?
- Using a digital multimeter, measure all resistors to three significant figures.

PART 4: POST-MEASUREMENT EXERCISE

- Calculate the values of V_{GS} and V_{DS} that you obtained in the lab. How do they compare to your pre-lab calculations? Explain any discrepancies.
- Based on the measured values of V_D and V_S and your measured resistor values, what is the real value of I_D based on your lab measurements?
- What is the measured value of A_v ? How does it compare to your pre-lab calculations? Explain any discrepancies.

- *Hint:* The single biggest source of variations from your pre-lab simulation results will be due to variations in the transistor threshold voltage V_{th} . Remember: Its value will be somewhere within the range indicated on the transistor datasheet.