

ENGR 305 Lab 9: Amplifier Schematics

Sean Balbale

November 6, 2025

1 Part 1: LTspice Simulation Schematic

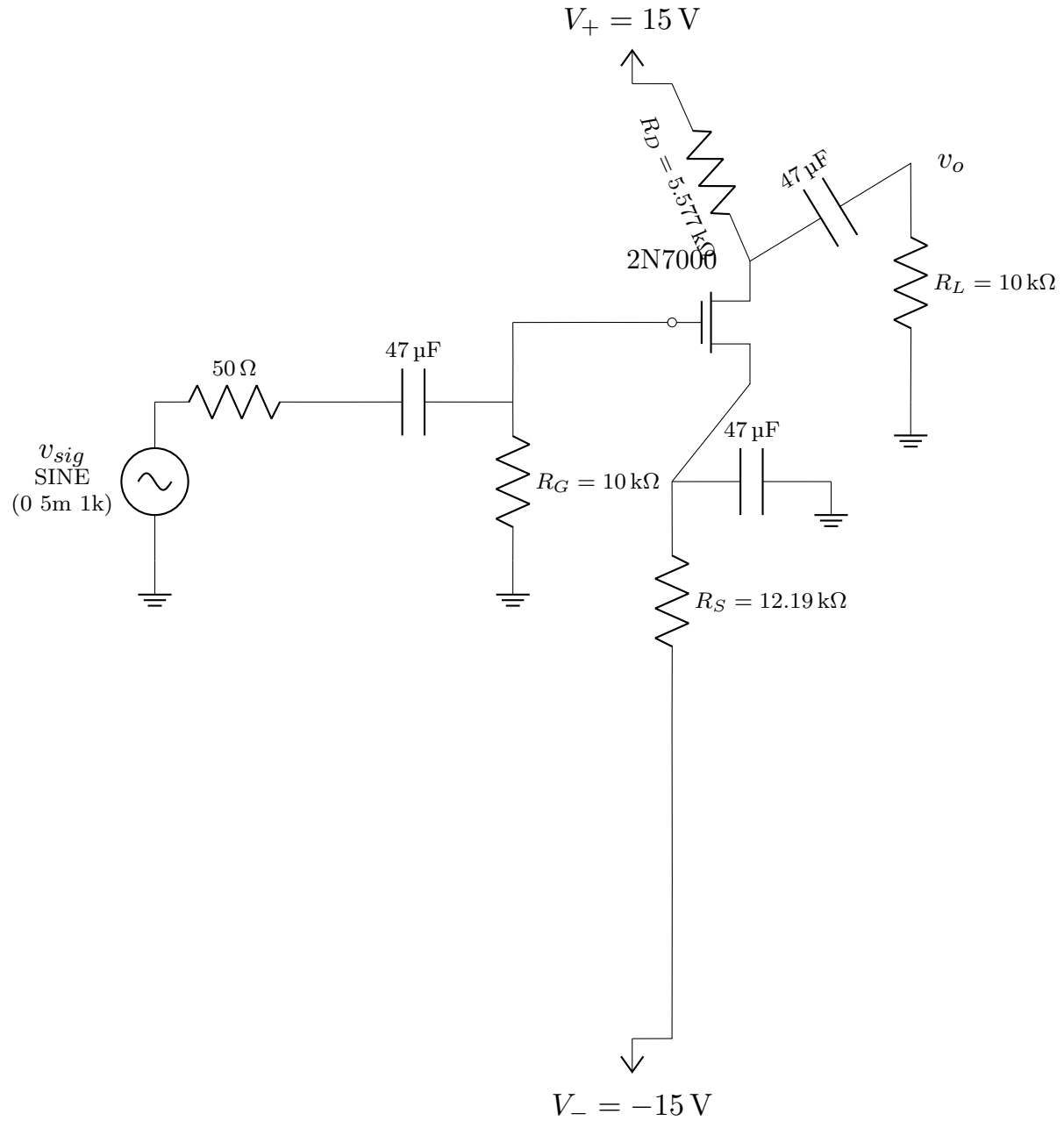


Figure 1: Schematic for LTspice simulation. This circuit includes the signal source v_{sig} and its internal resistance R_{sig} . It uses the exact calculated resistor values for R_D and R_S to verify the hand calculations.

2 Part 2: Physical Build Schematic

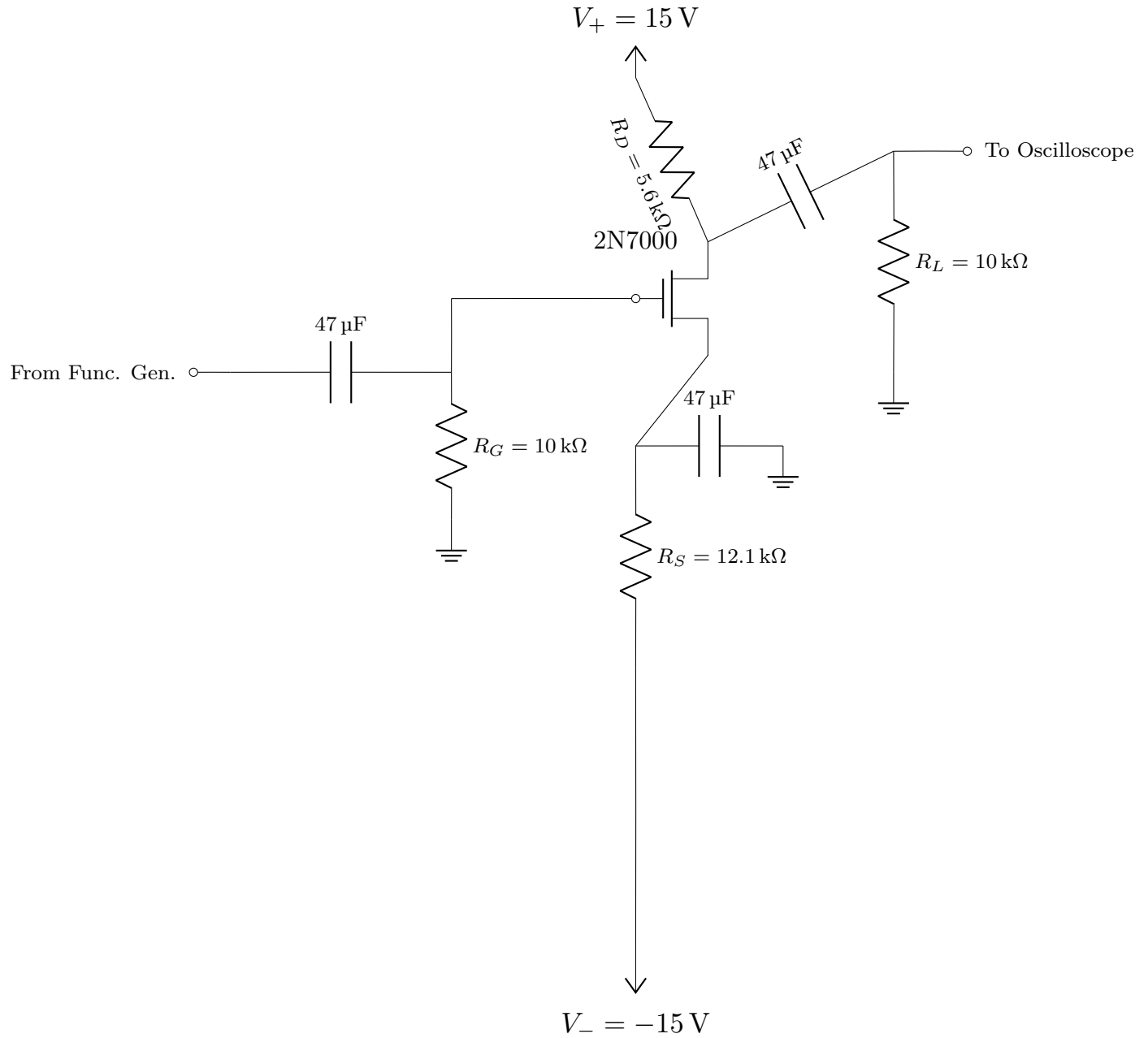


Figure 2: Schematic for physical breadboard implementation. R_{sig} is not included as it is internal to the function generator. Standard resistor values ($5.6\text{ k}\Omega$, $12.1\text{ k}\Omega$) are used for R_D and R_S .

3 AC Small-Signal Model Schematics

These diagrams show the equivalent circuit used for AC analysis, after all DC sources are grounded and all capacitors are treated as short circuits.

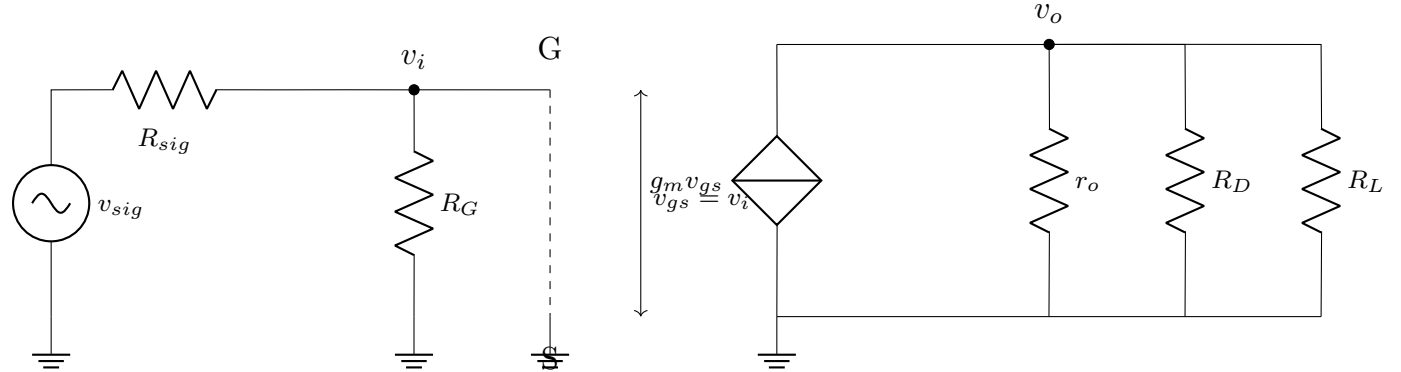


Figure 3: AC Small-Signal Model (Hybrid- π Model) showing all parallel output resistances.

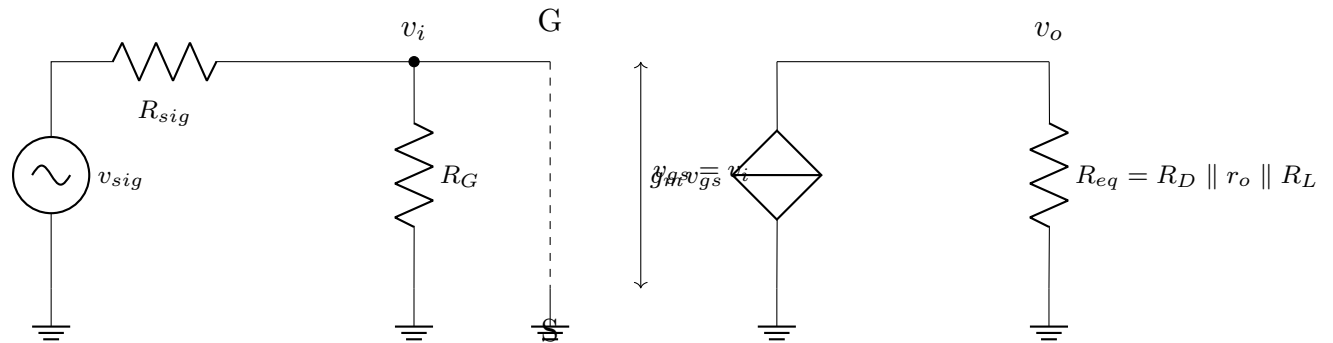


Figure 4: Simplified AC Small-Signal Model, with all output resistances combined into R_{eq} .