

ENGR 305 Lab 9: NMOS Common-Source Amplifier Hand Calculations

Sean Balbale

November 6, 2025

1 Part 1: Design and Simulation

1.1 Given Parameters and Design Goals

- **Voltage Supplies:** $V_+ = 15\text{ V}$, $V_- = -15\text{ V}$
- **Design Goals:** $I_D = 1\text{ mA}$, $A_v \leq -5\text{ V/V}$
- **Circuit Resistors:** $R_{sig} = 50\text{ }\Omega$, $R_L = 10\text{ k}\Omega$, $R_G = 10\text{ k}\Omega$
- **Transistor Parameters (2N7000):** $\lambda = 0.0146\text{ V}^{-1}$, $k_n = 1.08\text{ mA V}^{-2}$, $V_{tn} = 1.45\text{ V}$

1.2 DC Operating Point Analysis

 


Figure 1: DC Model of the Common-Source Amplifier

1. DC Gate Current and Voltage (I_G , V_G)

The DC gate current I_G for a MOSFET is effectively 0 A. The lab manual specifies a gate resistor R_G . Assuming R_G connects the gate to ground, the DC voltage drop across it is $I_G \cdot R_G = 0$ V. Therefore, the DC gate voltage is $V_G = 0$ V.

2. Overdrive Voltage (V_{OV})

Using the saturation current equation for the design goal $I_D = 1$ mA:

$$I_D = \frac{1}{2}k_n(V_{OV})^2$$

$$1 \text{ mA} = \frac{1}{2}(1.08 \text{ mA V}^{-2})(V_{OV})^2$$

$$V_{OV}^2 = \frac{2 \text{ mA}}{1.08 \text{ mA V}^{-2}} \approx 1.8519 \text{ V}^2$$

$$V_{OV} = \sqrt{1.8519 \text{ V}^2} \approx 1.361 \text{ V}$$

3. Transconductance (g_m) and Gate-Source Voltage (V_{GS})

The transconductance g_m is:

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \cdot 1 \text{ mA}}{1.361 \text{ V}} \approx 1.4695 \text{ mA V}^{-1} \text{ (or } 1.47 \text{ mS)}$$

The gate-source voltage V_{GS} is:

$$V_{GS} = V_{OV} + V_{tn} = 1.361 \text{ V} + 1.45 \text{ V} = 2.811 \text{ V}$$

4. Early Effect Resistance (r_o)

The output resistance of the transistor itself is:

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.0146 \text{ V}^{-1})(1 \text{ mA})} = \frac{1}{0.0000146 \text{ S}} \approx 68\,493 \, \Omega \text{ or } 68.5 \text{ k}\Omega$$

5. Source Resistor (R_S)

First, we find the DC source voltage V_S using $V_G = 0 \text{ V}$:

$$V_{GS} = V_G - V_S \implies 2.811 \text{ V} = 0 \text{ V} - V_S \implies V_S = -2.811 \text{ V}$$

The resistor R_S connects the source terminal (V_S) to the negative supply ($V_- = -15 \text{ V}$). The DC current through R_S is $I_S = I_D = 1 \text{ mA}$ (since $I_G = 0$).

$$R_S = \frac{V_S - V_-}{I_D} = \frac{-2.811 \text{ V} - (-15 \text{ V})}{1 \text{ mA}} = \frac{12.189 \text{ V}}{1 \text{ mA}} = 12.19 \text{ k}\Omega$$

This value is very close to the standard E24 resistor value of $12.1 \text{ k}\Omega$.

1.3 AC Analysis

For the AC model, all capacitors (C_{C1} , C_{C2} , C_S) are treated as short circuits, and DC supplies (V_+ , V_-) are treated as AC ground.

 


Figure 2: AC Small-Signal Model of the Common-Source Amplifier

1. Input Voltage Ratio (v_i/v_{sig})

The AC input resistance R_{in} of the amplifier is R_G in parallel with the gate's infinite resistance, so $R_{in} = R_G = 10 \text{ k}\Omega$. This forms a voltage divider with the signal source resistance R_{sig} .

$$\frac{v_i}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} = \frac{R_G}{R_{sig} + R_G} = \frac{10\,000\,\Omega}{50\,\Omega + 10\,000\,\Omega} = \frac{10000}{10050} \approx 0.995$$

This ratio is very close to 1, so for further calculations, we can approximate $v_i \approx v_{sig}$.

2. Drain Resistor (R_D) for Gain $A_v = -5 \text{ V/V}$

The AC bypass capacitor C_S shorts R_S to ground, so the source is at AC ground. The small-signal voltage gain $A_v = v_o/v_i$ is:

$$A_v = -g_m(r_o \parallel R_D \parallel R_L)$$

We need to solve for R_D to achieve $A_v = -5 \text{ V/V}$.

$$-5 \text{ V/V} = -(1.4695 \text{ mS})(68.5 \text{ k}\Omega \parallel R_D \parallel 10 \text{ k}\Omega)$$

First, let's combine the known parallel resistances $R'_L = r_o \parallel R_L$:

$$R'_L = \frac{68.5 \text{ k}\Omega \cdot 10 \text{ k}\Omega}{68.5 \text{ k}\Omega + 10 \text{ k}\Omega} = \frac{685}{78.5} \approx 8.726 \text{ k}\Omega$$

Now substitute this back into the gain equation:

$$5 = (1.4695 \text{ mS})(R_D \parallel 8.726 \text{ k}\Omega)$$

Let $R_{eq} = R_D \parallel 8.726 \text{ k}\Omega$. We solve for this equivalent resistance:

$$R_{eq} = \frac{5}{1.4695 \text{ mS}} \approx 3.4025 \text{ k}\Omega$$

Now, we can solve for R_D :

$$\frac{1}{R_{eq}} = \frac{1}{R_D} + \frac{1}{R'_L} \implies \frac{1}{R_D} = \frac{1}{R_{eq}} - \frac{1}{R'_L}$$

$$\frac{1}{R_D} = \frac{1}{3.4025 \text{ k}\Omega} - \frac{1}{8.726 \text{ k}\Omega} \approx 0.0002939 - 0.0001146 = 0.0001793 \text{ k}\Omega^{-1}$$

$$R_D = \frac{1}{0.0001793} \approx 5.577 \text{ k}\Omega$$

A standard 5.6 k Ω resistor would be a suitable choice.

3. DC Drain Voltage (V_D) and Saturation Check

Using our calculated $R_D = 5.577 \text{ k}\Omega$, we find the DC drain voltage V_D :

$$V_D = V_+ - I_D R_D = 15 \text{ V} - (1 \text{ mA})(5.577 \text{ k}\Omega) = 15 \text{ V} - 5.577 \text{ V} = 9.423 \text{ V}$$

To be in saturation, the transistor must satisfy $V_{DS} \geq V_{OV}$.

$$V_{DS} = V_D - V_S = 9.423 \text{ V} - (-2.811 \text{ V}) = 12.234 \text{ V}$$

Check: $V_{DS}(12.234 \text{ V}) \geq V_{OV}(1.361 \text{ V})$. The condition is clearly met, so the transistor is operating in the saturation region as assumed.

4. Amplifier Output Resistance (R_o)

The output resistance R_o of the amplifier (as defined in the lab manual, step 2) is the resistance looking into the drain, *before* R_L is attached. This is R_D in parallel with r_o .

$$R_o = R_D \parallel r_o = 5.577 \text{ k}\Omega \parallel 68.5 \text{ k}\Omega$$

$$R_o = \frac{5.577 \text{ k}\Omega \cdot 68.5 \text{ k}\Omega}{5.577 \text{ k}\Omega + 68.5 \text{ k}\Omega} = \frac{381.99}{74.077} \approx 5.157 \text{ k}\Omega$$

2 Summary of Calculated Values

The following table summarizes all the key calculated values from the design and analysis of the NMOS common-source amplifier:

Table 1: Summary of Calculated Design Parameters			
Parameter	Symbol	Value	Section
<i>DC Operating Point</i>			
DC Gate Current	I_G	0 A	1.2
DC Gate Voltage	V_G	0 V	1.2
Overdrive Voltage	V_{OV}	1.361 V	1.2
Transconductance	g_m	1.47 mS	1.2
Gate-Source Voltage	V_{GS}	2.811 V	1.2
Early Effect Resistance	r_o	68.5 k Ω	1.2
DC Source Voltage	V_S	-2.811 V	1.2
Source Resistor	R_S	12.19 k Ω	1.2
<i>AC Analysis and Design</i>			
Input Voltage Ratio	v_i/v_{sig}	0.995	1.3
Drain Resistor	R_D	5.577 k Ω	1.3
DC Drain Voltage	V_D	9.423 V	1.3
Drain-Source Voltage	V_{DS}	12.234 V	1.3
Voltage Gain	A_v	-5 V/V	1.3
Output Resistance	R_o	5.157 k Ω	1.3
<i>Design Goals & Given Parameters</i>			
Drain Current (Design)	I_D	1 mA	1.1
Positive Supply	V_+	15 V	1.1
Negative Supply	V_-	-15 V	1.1
Signal Source Resistance	R_{sig}	50 Ω	1.1
Load Resistance	R_L	10 k Ω	1.1
Gate Resistance	R_G	10 k Ω	1.1
Channel-Length Modulation	λ	0.0146 V ⁻¹	1.1
Transconductance Parameter	k_n	1.08 mA V ⁻²	1.1
Threshold Voltage	V_{tn}	1.45 V	1.1

Note: The transistor is confirmed to be in saturation since $V_{DS} = 12.234 \text{ V} \geq V_{OV} = 1.361 \text{ V}$.