

ENGR 305 Lab 10: Hand Calculations

Sean Balbale

November 19, 2025

1 Part 1: Design and DC Analysis

1.1 Given Parameters

- **Supplies:** $V_+ = 15\text{ V}$, $V_- = -15\text{ V}$
- **Design Goals:** $I_C = 1\text{ mA}$, Gain $A_v = -200\text{ V/V}$
- **Components:** $R_{sig} = 50\ \Omega$, $R_L = 10\text{ k}\Omega$, $R_B = 10\text{ k}\Omega$
- **Transistor Model:** 2N3904 NPN, assume $\beta = 100$, $V_{BE} = 0.7\text{ V}$, $V_T \approx 26\text{ mV}$

1.2 DC Operating Point Analysis

For the DC analysis, all coupling capacitors (C_{c1}, C_{c2}) and bypass capacitors (C_E) are treated as open circuits. The base is connected to ground through R_B .

 


Figure 1: DC Equivalent Circuit

1. Calculate Base and Emitter Currents (I_B, I_E)

Using the target collector current $I_C = 1 \text{ mA}$ and $\beta = 100$:

$$I_B = \frac{I_C}{\beta} = \frac{1 \text{ mA}}{100} = 10 \mu\text{A}$$

$$I_E = I_C + I_B = 1 \text{ mA} + 0.01 \text{ mA} = 1.01 \text{ mA}$$

2. Calculate Base and Emitter Voltages (V_B, V_E)

The base current flows from ground, through R_B , into the base.

$$V_B = 0 - I_B R_B = 0 - (10 \mu\text{A})(10 \text{ k}\Omega) = -0.1 \text{ V}$$

Using the standard assumption of a 0.7 V drop across the base-emitter junction:

$$V_E = V_B - V_{BE} = -0.1 \text{ V} - 0.7 \text{ V} = -0.8 \text{ V}$$

3. Design Emitter Resistor (R_E)

R_E sets the bias current. It is calculated from the voltage drop across it ($V_E - V_-$) and I_E .

$$R_E = \frac{V_E - V_-}{I_E} = \frac{-0.8 \text{ V} - (-15 \text{ V})}{1.01 \text{ mA}} = \frac{14.2 \text{ V}}{1.01 \text{ mA}} \approx 14.06 \text{ k}\Omega$$

Practical Note: $14.06 \text{ k}\Omega$ is not a standard E12/E24 value. It can be approximated using a decade box or a series combination (e.g., $10 \text{ k}\Omega + 3.9 \text{ k}\Omega + 160 \Omega$).

2 Part 2: AC Small-Signal Analysis

2.1 Small-Signal Parameters

First, we calculate the transconductance (g_m) and input resistance (r_π) using the thermal voltage $V_T \approx 26 \text{ mV}$:

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} \approx 38.46 \text{ mS}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{38.46 \text{ mS}} \approx 2.6 \text{ k}\Omega$$

2.2 Circuit Model

In the small-signal analysis, DC supplies become AC grounds, and large capacitors act as short circuits. The emitter resistor R_E is bypassed by C_E , connecting the emitter directly to ground.

 


Figure 2: Small-Signal Model (Hybrid- π)

2.3 Gain Derivation and Design

1. Voltage Gain Expression (A_v)

The output voltage is generated by the dependent current source pulling current through the parallel combination of R_C and R_L :

$$v_o = -(g_m v_\pi)(R_C || R_L)$$

Since $v_\pi = v_i$ (emitter is grounded), the gain A_v is:

$$A_v = \frac{v_o}{v_i} = -g_m(R_C || R_L)$$

2. Design Collector Resistor (R_C)

We require a gain of $A_v = -200$.

$$|-200| = g_m(R_C || R_L) \implies 200 = (38.46 \text{ mS}) \left(\frac{R_C R_L}{R_C + R_L} \right)$$

Solving for the equivalent resistance $R_{eq} = R_C || R_L$:

$$R_{eq} = \frac{200}{38.46 \text{ mS}} \approx 5.2 \text{ k}\Omega$$

Now solve for R_C knowing $R_L = 10 \text{ k}\Omega$:

$$\begin{aligned} \frac{1}{R_{eq}} &= \frac{1}{R_C} + \frac{1}{R_L} \implies \frac{1}{R_C} = \frac{1}{5.2 \text{ k}\Omega} - \frac{1}{10 \text{ k}\Omega} \\ \frac{1}{R_C} &\approx 1.923 \times 10^{-4} - 1 \times 10^{-4} = 0.923 \times 10^{-4} \text{ S} \\ R_C &\approx 10.83 \text{ k}\Omega \end{aligned}$$

Practical Note: This can be implemented with a $10 \text{ k}\Omega$ and an 820Ω resistor in series, or using a decade box.

2.4 Verification and Analysis

1. DC Collector Voltage (V_C)

We must verify the transistor remains in the active region ($V_C > V_B$).

$$V_C = V_+ - I_C R_C = 15 \text{ V} - (1 \text{ mA})(10.83 \text{ k}\Omega) = 15 \text{ V} - 10.83 \text{ V} = 4.17 \text{ V}$$

Since $V_C(4.17 \text{ V}) > V_B(-0.1 \text{ V})$, the transistor is in the Active Region.

2. Output Resistance (R_o)

The output resistance looking into the collector is approximately R_C (ignoring the transistor's early voltage V_A).

$$R_o \approx R_C = 10.83 \text{ k}\Omega$$

3. Input Attenuation (v_i/v_{sig})

The input impedance Z_{in} looking into the base is $R_B || r_\pi$:

$$Z_{in} = \frac{R_B r_\pi}{R_B + r_\pi} = \frac{10 \cdot 2.6}{10 + 2.6} \text{ k}\Omega \approx 2.06 \text{ k}\Omega$$

The signal reaching the base v_i is a voltage divider with $R_{sig} = 50\ \Omega$:

$$\frac{v_i}{v_{sig}} = \frac{Z_{in}}{Z_{in} + R_{sig}} = \frac{2060\ \Omega}{2060\ \Omega + 50\ \Omega} \approx 0.976$$

This is close to unity, so the overall system gain is approximately equal to the stage gain A_v .

3 Summary of Values

The following table summarizes all assumed, given, and calculated values used in this lab analysis.

Table 1: Summary of Circuit Parameters		
Parameter	Symbol	Value
<i>Given & Assumed Constants</i>		
Positive Supply Voltage	V_+	15 V
Negative Supply Voltage	V_-	-15 V
Target Collector Current	I_C	1 mA
Transistor Beta	β	100
Base-Emitter Voltage	V_{BE}	0.7 V
Thermal Voltage	V_T	26 mV
Signal Source Resistance	R_{sig}	50 Ω
Load Resistance	R_L	10 k Ω
Base Bias Resistor	R_B	10 k Ω
Target Gain	A_v	-200 V/V
<i>Calculated DC Values</i>		
Base Current	I_B	10 μ A
Emitter Current	I_E	1.01 mA
Base Voltage	V_B	-0.1 V
Emitter Voltage	V_E	-0.8 V
Emitter Resistor (Calculated)	R_E	14.06 k Ω
Collector Resistor (Calculated)	R_C	10.83 k Ω
Collector Voltage	V_C	4.17 V
<i>Calculated AC Values</i>		
Transconductance	g_m	38.46 mS
Input Resistance (Base)	r_π	2.6 k Ω
Input Impedance (Total)	Z_{in}	2.06 k Ω
Output Resistance	R_o	10.83 k Ω
Input Attenuation Ratio	v_i/v_{sig}	0.976